

# The effect of Pull Up Resistance and Load Capacitance to $R/\bar{B}$ pin's slope

SEP. 30<sup>th</sup>, 2005

Product Planning & Application Engineering Team

MEMORY DIVISION  
SAMSUNG ELECTRONICS Co., LTD

# R/ $\bar{B}$ pin's application

## □ Indicates the internal controller operation

- Indicating the completion of a page program, erase, random read, and read (at 128KB block sized NAND) operation.

### 1. High state : Normal mode


- Ready for operation
- Completion of operation

### 2. Low state : Busy mode

- After the program or erase or read command is written to the command register
- Random read is started after address loading.
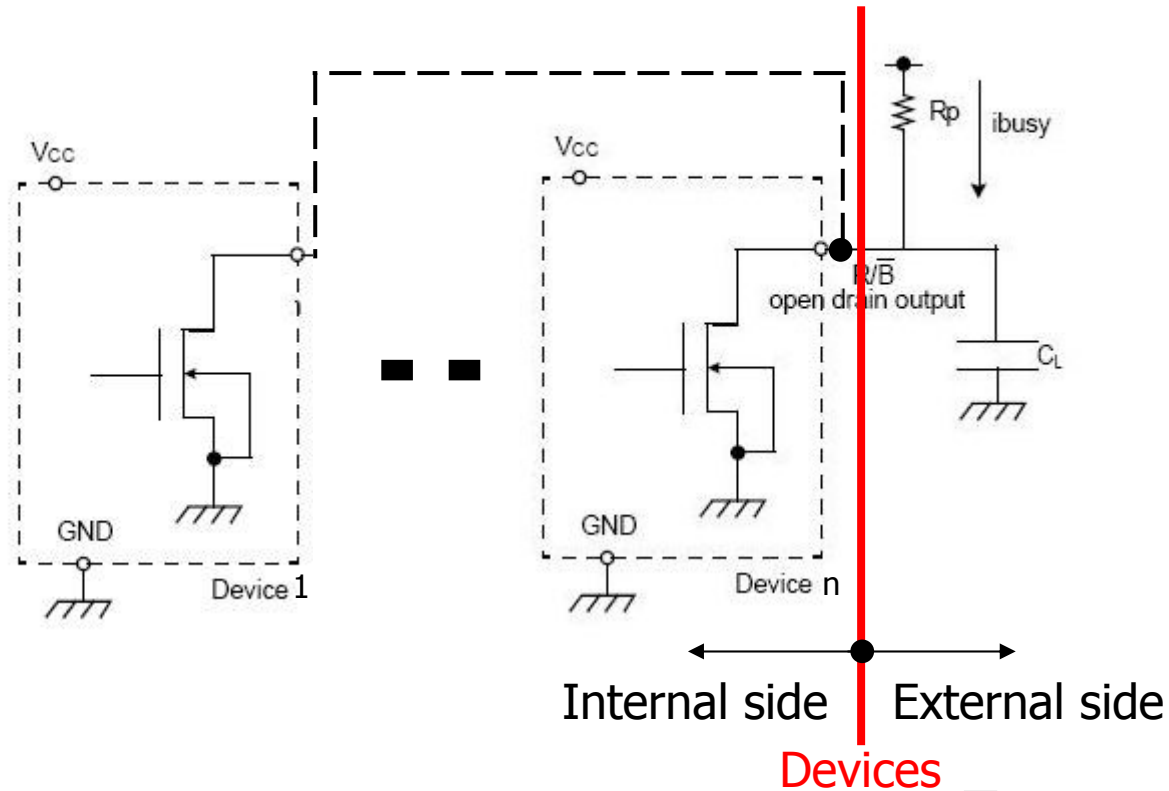
# Circuit Diagram of $R/\bar{B}$ pin


- Two or more  $R/\bar{B}$  outputs to be OR-tied



- In case of Multi-chip package, more than one  $R/\bar{B}$  would be connected.
- Or-Tied means if one or more of devices are busy state, then the output of  $R/\bar{B}$  will be LOW state (busy state).
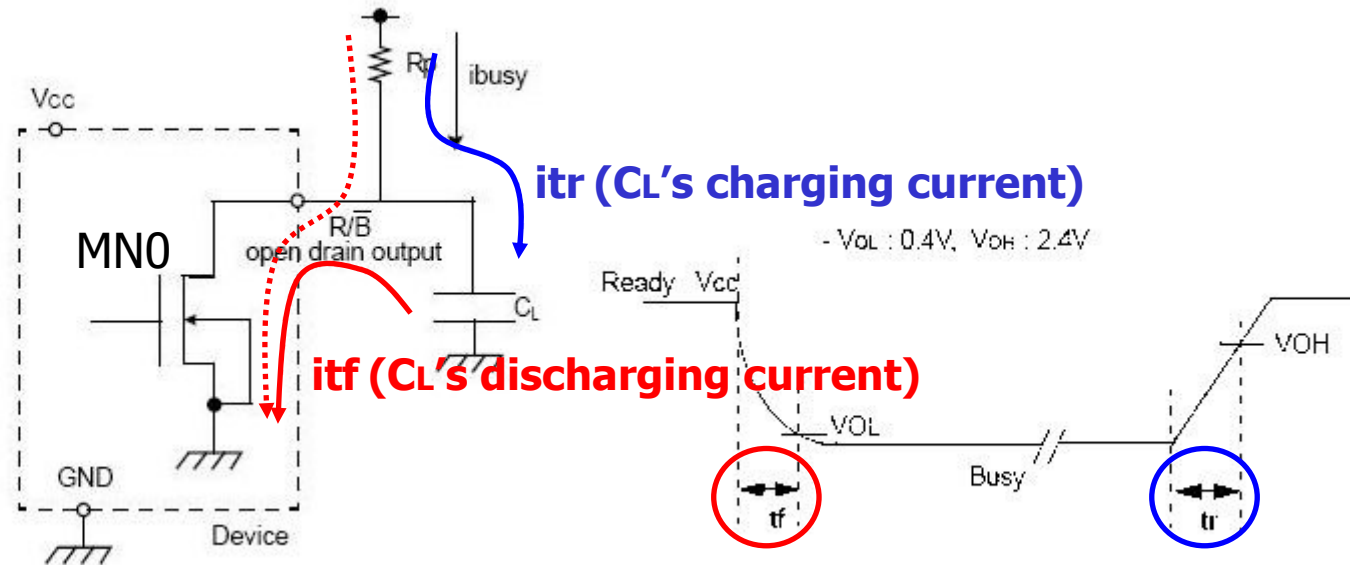
# Relationship with Signal slope

- Time of falling and rising are related to  $R_p$ , and  $C_L$




- $t_f$  is controlled by MN0's current driving ability
  - The driving ability of MN0 transistor is assumed to be sufficient enough to drive  $t_f$  as rapidly as expected
  - $I_{busy}$  electric current also affects the  $t_f$ , but the level may be not so good to compare to Charged electric charge in the load capacitor  $C_L$

# Simple description about tr

## □ The relation of slope time, Rp, and Ibusy

- Guided by specification of K9F2G08U0M

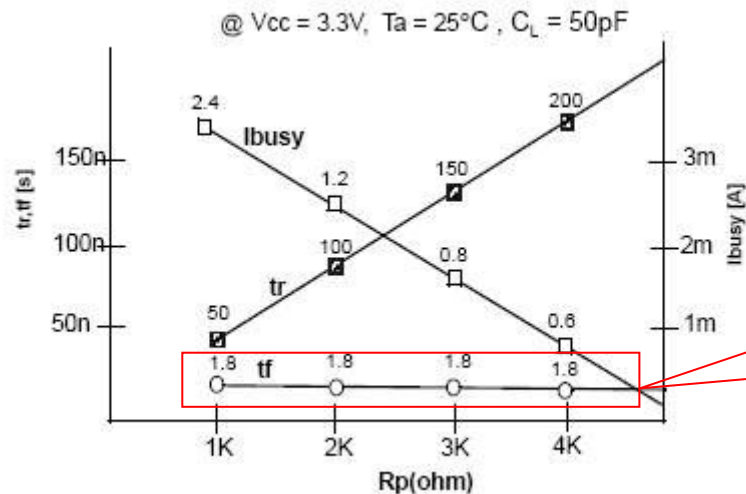

tf seems to be unchanged with pull up resistor by MNO's strong current driving ability

## □ itr is controlled by Rp's value (assumed that CL is constant)

- $\Delta q$  (electric charge quantity variation) =  $i$  ( electric current ) \*  $\Delta t$  (time variation)
- $V$  (voltage) =  $I$  (electric current) \*  $R$  (resistance value)

1.  $i_{tr}$  (electric current) may be inverse proportion relation to  $tr$  (charging time)
2.  $I$  (electric current) is inverse proportion relation to  $R$  (resistance value)

## □ The relationship of tr with electric current, and pull up resistor from above figure

- $I_1 * tr_1 = I_2 * tr_2 = I_3 * tr_3 = I_4 * tr_4$  (changing Rp affects Ibusy)
  - $2.4mA * 50ns = 1.2mA * 100ns = 0.8mA * 150ns = 0.6mA * 200ns$
- $tr_1 \propto Rp_1, tr_2 \propto Rp_2, tr_3 \propto Rp_3, tr_4 \propto Rp_4$ 
  - $50ns \propto 1K, 100ns \propto 2K, 150ns \propto 3K, 200ns \propto 4K$

# Simple description about Ibusy

## □ The switch-on resistance ( $R_{on}$ ) value of MN0 (at page 4)

- Its value is SMALL enough TO be IGNORED in comparison to  $R_p$
- The resistance value of the path of Vcc to GND is  $R_p + R_{on}$  (expect  $20\Omega$ )
  - But,  $R_{on} \ll R_p$  means
    - $R_p + R_{on} \approx R_p$
  - **So, the resistance value of the path of Vcc to GND is about  $R_p$**

## □ By the Ohm's Law

- $V_{OH} = I_{busy} * R_p$ 
  - Reference voltage is  $V_{OH}$  (2.4V)
- In case of  $R_p$ 
  - $R_p = 1K\Omega / 2K\Omega / 3K\Omega / 4K\Omega$ 
    - $V_{OH}(2.4V) = I_{busy} * R_p$
    - $I_{busy} = 2.4mA / 1.2mA / 0.8mA / 0.6mA$

# Simple expectation of CL change

□  $V = I * R$  (Ohm's Law)

- If Voltage V and resistance value R are not changed, then electric current I is not changed.

□  $Q = I * T$  (Preservation Law of Electric charge quantity)


- Additionally,  $Q$  (electric charge quantity) =  $C$  (Capacitance) \*  $V$  (Voltage)
- The  $C$  value is directly proportional to the  $I$  value
  - $Q = C * V = I * T$ 
    - If  $V$  and  $I$  are not changed, then  $C$  is directly proportional to  $T$
- Case of  $R_p = 1K\Omega$ 
  1. If  $C$  is decreased to 5 times ( $C_L = 10pF$ , referred to the figure of page 5), then **tr will be decreased to 5 times (tr ≈ 10ns)**
  2. If  $C$  is increased to 5 times ( $C_L = 250pF$ ), then **tr will be increased to 5 times (tr ≈ 250ns)**
    - \* *The value of tr ≈ 250ns may be the same result of  $C_L=50pF$ ,  $R_p = 5K\Omega$*

□  $\tau = C * R$


- The rising time is directly calculated by this equation

# Test environment

## □ Top view

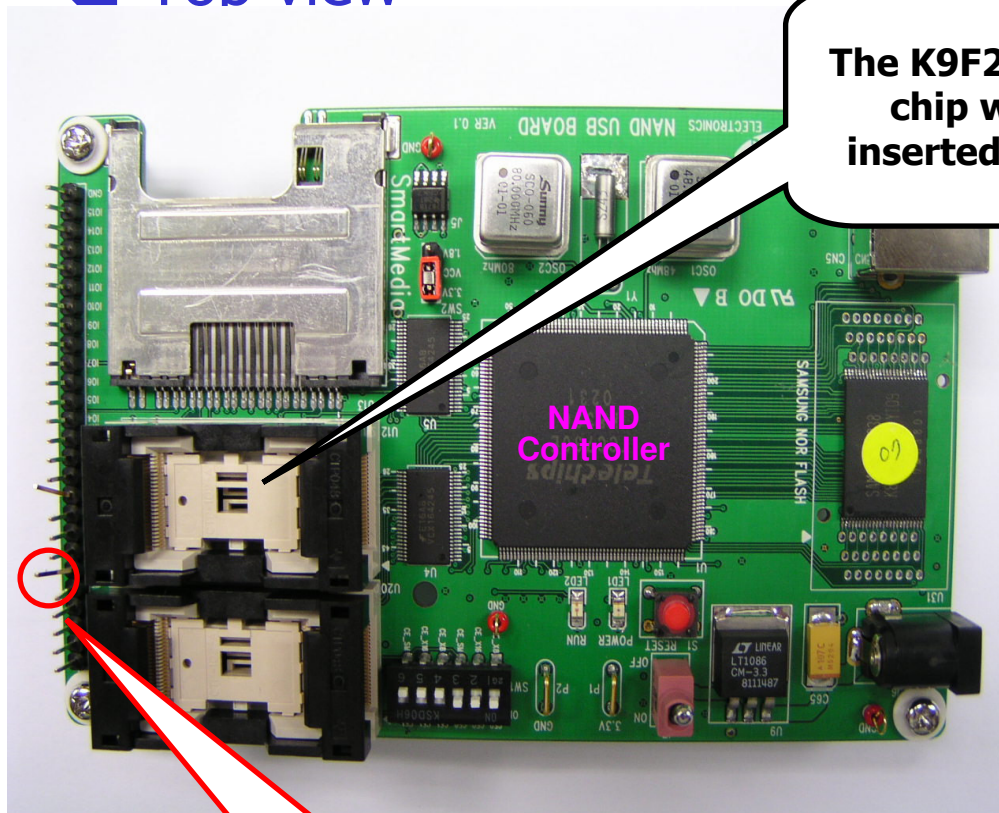

## □ Bottom view

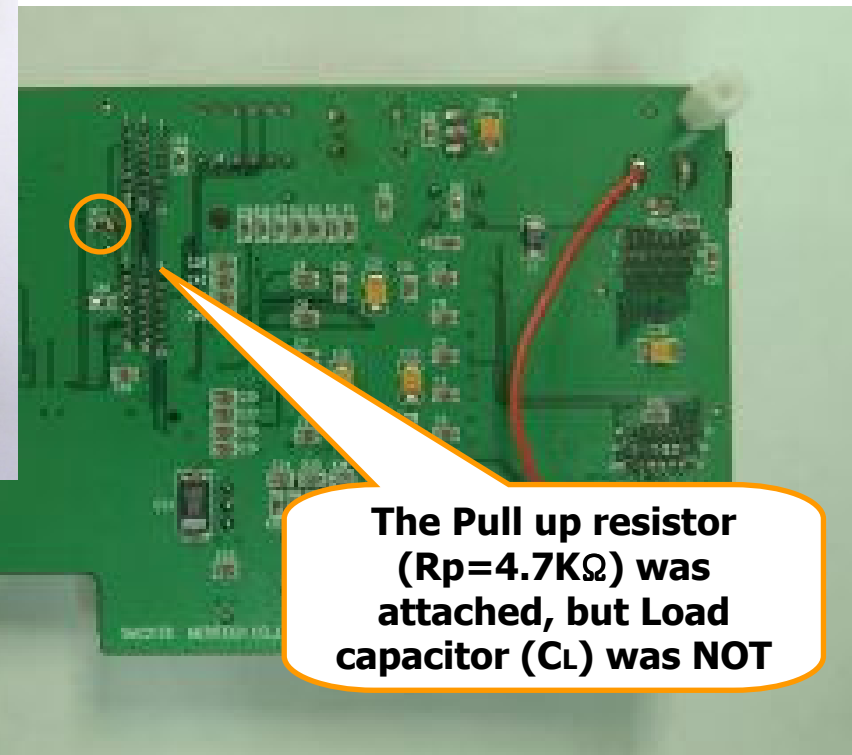


# Test result of $t_f$ , $t_r$ with $R_p$ , $C_L$ change

Change of  $R_p$ , and  $C_L$  (at K9F2G08U0M)

$t_f$  :  $V_{CC}$  to  $V_{OL}(0.4V)$   
 $t_r$  :  $GND$  to  $V_{OH}(2.4V)$

	Additional Load Cap.	$R_p$				
		1.57K $\Omega$	1.90K $\Omega$	2.35K $\Omega$	3.20K $\Omega$	4.7K
$t_f$		1ns	1ns	1ns	1ns	1ns
$t_{r1}$	18pF	104ns	128ns	162ns	218ns	322ns
$t_{r2}$	68pF	207ns	244ns	310ns	420ns	616ns
$t_{r3}$	118pF	294ns	374ns	452ns	604ns	928ns
$t_{r4}$	168pF	392ns	484ns	588ns	832ns	1190ns

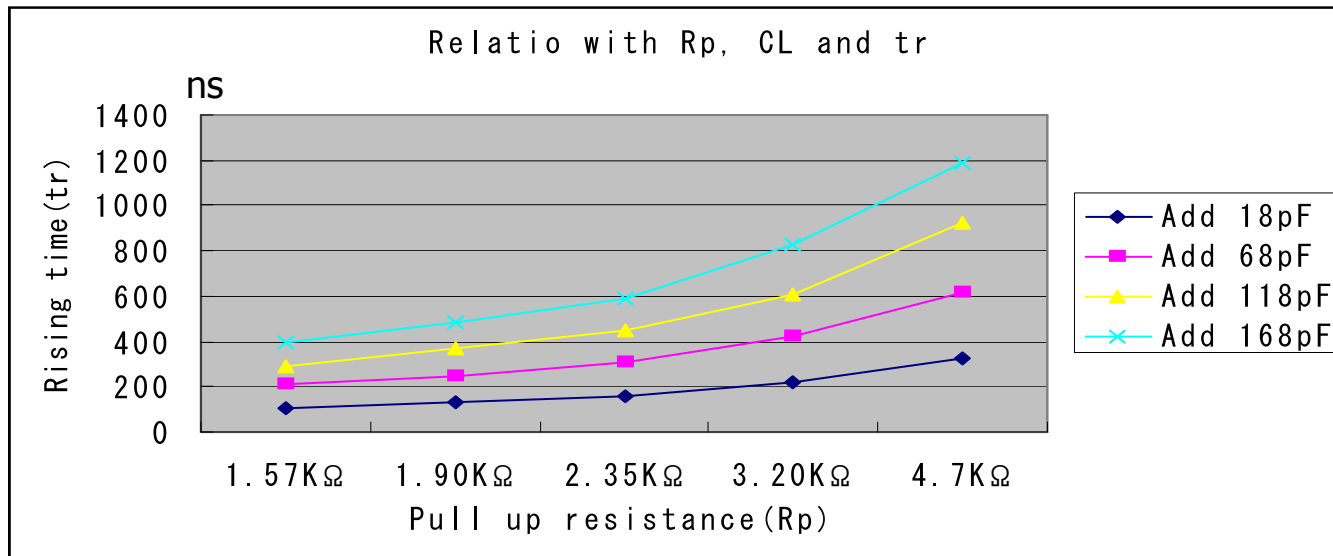

# Test result analysis

## ❑ Expect Initial Load Cap. by previous table

- By the tr1 with the condition of 4.7KΩ of pull up resistor
  - $tr_{4.7K\Omega} = (C_{init} + 18pF) * 4.7K\Omega = 322ns$
  - $C_{init} = 50pF$

## ❑ Measure initial load capacitance

- By HP4284A equipment
  - Which measures the initial load capacitance and initial resistance of node, etc
- The R/B's initial load capacitance is 67pF
  - This shows that the tr<sub>67pF</sub> of 4.7KΩ's pull up resistor must have longer time than measured value(322ns)
    - $322ns : X = 50pF : 67pF$
    - **X = 399ns**
  - At the tr2

	1.57K	1.9K	2.35K	3.2K	4.7K
Measured	207ns	244ns	310ns	420ns	616ns
Expected	201ns	243ns	300ns	409ns	601ns

## ❑ The difference of expect and measure

- All of passive devices have the error rate (about 10%) even the measurement equipment
- May be the error rate of each device affects the difference including Human Error.
- But, at the tr2 the expected value and the measured value are nearly same.